

# Lab Report5

## 1. ALU

 


Fig 1.1 ALU

### 1.1 Test Result

 


Fig 1.2 ALU test result

- SRL 0xFFFF1234,6 passed
- ADDU 0,0 passed
- ADDU 0,-1 passed
- ADDU -1,0 passed
- ADDU FF,1 passed
- SUBU 0,0 passed
- SUBU 1,-1 passed
- SUBU 1,1 passed
- XOR 0xF0F0F0F0,0x0000FFFF passed
- XOR 0x12345678,0x87654321 passed
- SLTU 0,0 passed
- SLTU 0,1 passed
- SLTU 0,-1 passed
- SLTU 1,0 passed
- SLTU -1,0 passed
- NOR 0xF0F0F0F0,0x0000FFFF passed
- NOR 0x12345678,0x87654321 passed
- SRA 0x00000001,3 passed
- SRA 0x00001234,6 passed
- SRA 0xFFFF1234,6 passed
- LUI 0x12345678 passed
- LUI 0x00001234 passed
- All tests passed

1.2 Synthesis Log

```
C:/Users/songz/lab5/lab5.runs/synth_2/ALU.vds
```

Q

warning

Next

Previous

Highlight

☐ Match Case

☐ Whole Words

7 Match(es)

```
137
138
139 Start Final Netlist Cleanup
140
141
142 Finished Final Netlist Cleanup
143
144
145 Finished IO Insertion : Time (s): cpu = 00:00:10 ; elapsed = 00:00:12 . Memory (MB): peak = 793.133 ; gain = 524.617
146
147
148 Report Check Netlist:
149 +-----+-----+-----+-----+-----+
150 |      |Item      |Errors |Warnings|Status |Description |
151 +-----+-----+-----+-----+-----+
152 |1     |multi_driven_nets |    0|    0|Passed |Multi driven nets |
153 +-----+-----+-----+-----+-----+
```

Fig 1.2 Synthesis Report

2. ALU Control

2.1 Synthesis Report

```
C:/Users/songz/lab5/lab5.runs/synth_2/ALUControl.vds
```

Q

Warning

Next

Previous

Highlight

☐ Match Case

☐ Whole Words

7 Match(es)

```
128
129
130 Finished Final Netlist Cleanup
131
132
133 Finished IO Insertion : Time (s): cpu = 00:00:07 ; elapsed = 00:00:08 . Memory (MB): peak = 733.598 ; gain = 465.344
134
135
136 Report Check Netlist:
137 +-----+-----+-----+-----+-----+
138 |      |Item      |Errors |Warnings|Status |Description |
139 +-----+-----+-----+-----+-----+
140 |1     |multi_driven_nets |    0|    0|Passed |Multi driven nets |
141 +-----+-----+-----+-----+-----+
142
143 Start Renaming Generated Instances
144
145
146 Finished Renaming Generated Instances : Time (s): cpu = 00:00:07 ; elapsed = 00:00:08 . Memory (MB): peak = 733.598 ; gain = 465.344
147
```

Fig 2.1 Synthesis Report

## 2.2 Test Result

SLL Instruction passed  
 SRL Instruction passed  
 SRA Instruction passed  
 ADD Instruction passed  
 ADDU Instruction passed  
 SUB Instruction passed  
 SUBU Instruction passed  
 AND Instruction passed  
 OR Instruction passed  
 XOR Instruction passed  
 NOR Instruction passed  
 SLT Instruction passed  
 SLTU Instruction passed  
 ANDI Instruction passed  
 ORI Instruction passed  
 ADDI Instruction passed  
 SUBI Instruction passed  
 SLTI Instruction passed  
 ADDIU Instruction passed  
 SUBIU Instruction passed  
 XORI Instruction passed  
 SLTIU Instruction passed  
 NORI Instruction passed  
 LUI Instruction passed  
 All tests passed

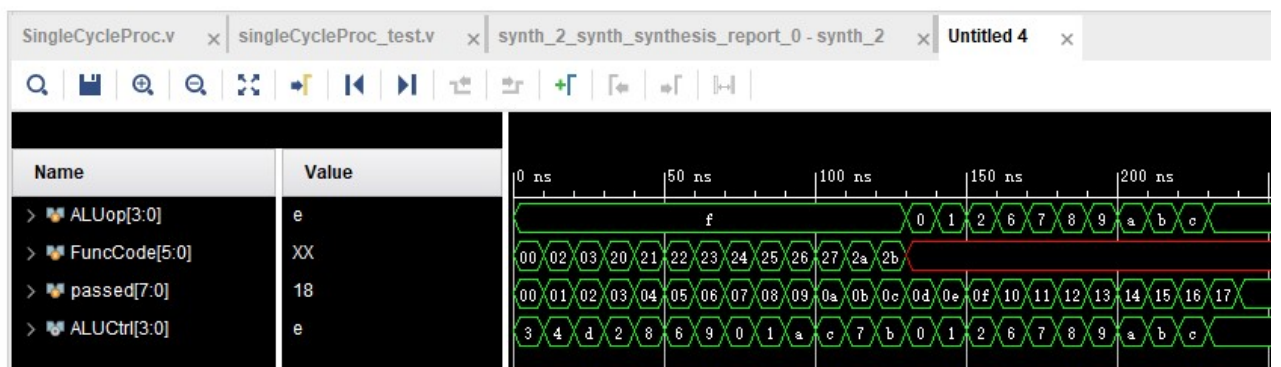


Fig 2.2 ALU Control Test Control

### 3. Single Cycle Control

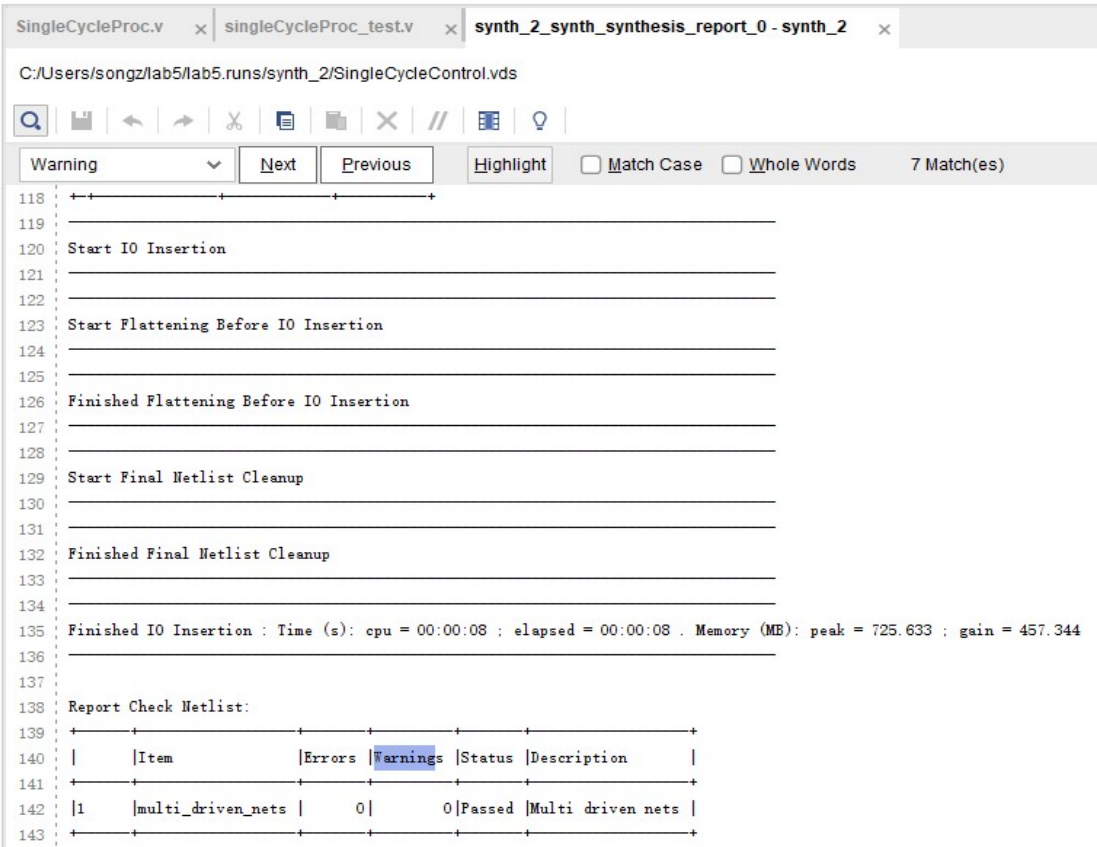


Fig 3.1 Synthesis Report

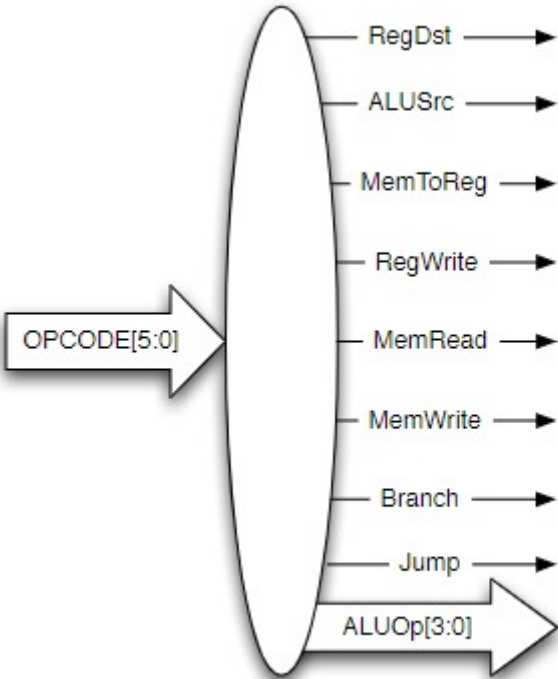


Fig 3.2 Single Cycle Controller Schematic

## 4. Single Cycle Processor

### 4.1 Synthesis Report

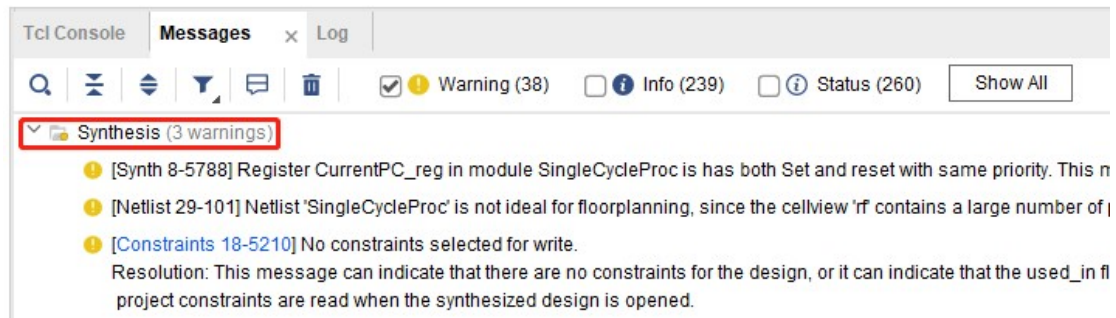


Fig 4.1 Synthesis Report

### 4.2 Test Result

 


Fig 4.2 Single Cycle Processor Waveform

```
run all

Results of Program 1 passed
Results of Program 2 passed
Result 1 of Program 3 passed
Result 2 of Program 3 passed
Result 3 of Program 3 passed
Result 4 of Program 3 passed
Result 5 of Program 3 passed
Result 6 of Program 3 passed
Result 7 of Program 3 passed
Result 8 of Program 3 passed
Result 9 of Program 3 passed
Result 10 of Program 3 passed
Result 11 of Program 3 passed
Result 12 of Program 3 passed

All tests passed
```

Fig 4.3 Output Log

## 5. Questions

(a) Explain why we designed the data memory such that reads happen on the positive edge of the clock, while writes happen on the negative edge of the clock.

Because address bus in reading, and writing bus in writing, are separate. In this way, memory read and write can happen in one cycle.

(b) Take a look at the test programs provided in the instruction memory Verilog file (only test pro-grams 1 through 3) and briefly explain what each of them do and what instructions they test.

Test program1: To sum a array whose starting address is \$a0, the size is \$a1. Use loop to sum words in array and store the sum.


Test program2: Do some arithmetic computations and store the final result into data memory address[32].

Test program3: Do some immediate numbers calculations, and store each result in different data memory addresses. At last, load each data.

(c) If you wanted to support the bne instruction, what modifications would you have to do to your design? Include changes to all affected sub-components as well.

First, ALU Control component needs to be modified, a new case for BNE should be added. Opcode is like BEQ case. Output of controller should add a wire of BNE. Plus the wire connections near final PC needs to be modified as well.

 (d) What clock rate did the synthesis process estimate your overall design would run at? Explain why this design is inefficient and provide suggestions for improvement.



Clk cycle is 120 ns. So clock rate is  $8.33 \times 10^6$  Hz. This rate is so low for a processor. Thus this single cycle is inefficient.